

CHAPTER 23 (CONT)

23.3 (CONT)

$$3V_{IH}^2 - 6V_{IH} - 3V_{IH} + 6 - 2\left(\frac{9}{16}V_{IH}^2 - \frac{9}{4}V_{IH} + \frac{9}{4}\right) = 16 - 8V_{IH} + V_{IH}^2$$

$$V_{IH}^2\left(3 - \frac{9}{8} - 1\right) + V_{IH}\left(-6 - 3 + \frac{9}{2} + 8\right) + \left(6 - \frac{9}{2} - 16\right) = 0$$

$$V_{IH}^2(0.875) + V_{IH}(3.5) - 14.5 = 0$$

$$V_{IH}^2 + 0.4V_{IH} - 16.6 = 0$$

$$\therefore V_{IH} = \frac{-0.4}{2} + \frac{\sqrt{(0.4)^2 + 4(16.6)}}{2} = -0.2 + 4.54 = 2.54V$$

V_M :

$$\begin{aligned} V_M &= \left[V_{DD} + V_{TP} + V_{TN} \sqrt{\frac{K_N}{K_P}} \right] / \left[1 + \sqrt{\frac{K_N}{K_P}} \right] \\ &= \left[5 + (-1) + 1 \sqrt{\frac{100}{50}} \right] / \left[1 + \sqrt{\frac{100}{50}} \right] = \frac{5.4142}{2.416} \\ &= 2.24V \end{aligned}$$

$$V_{NMH} = V_{OH} - V_{IH} = 5 - 2.54 = 2.46V$$

$$V_{NML} = V_{IL} - V_{OL} = 1.79 - 0 = 1.79V$$

23.4 GRAPHICAL DETERMINATION OF CRITICAL VOLTAGES

$$V_{DD} = 10V$$

$$I_{D,N}(SAT) = 50\mu(V_{IN} - 1)^2 \quad \text{UNCHANGED FROM PROBLEM 23.2}$$

$$I_{D,P}(SAT) = \frac{50}{2}(V_{GS,P} + V_T)^2 = 25\mu(10 - V_{IN} - 1)^2$$



$$I_{D,P}(SAT) = 25\mu(9 - V_{IN})^2$$

V_{IN}	$I_{D,N}(SAT)$	V_{IN}	$I_{D,P}(SAT) \text{ mA}$	$V_{SGP} = (10 - V_{IN})$
1	0	1	1.6	9
2	0.05	2	1.225	8
4	0.45	4	0.625	6
6	0.8	6	0.225	4
8	2.45	8	0.025	2
10	4.05	9	0	1 < V_T

IV CHARACTERISTICS
ON NEXT PAGE

CHAPTER 23 (CONT)

23.4 (CONT)

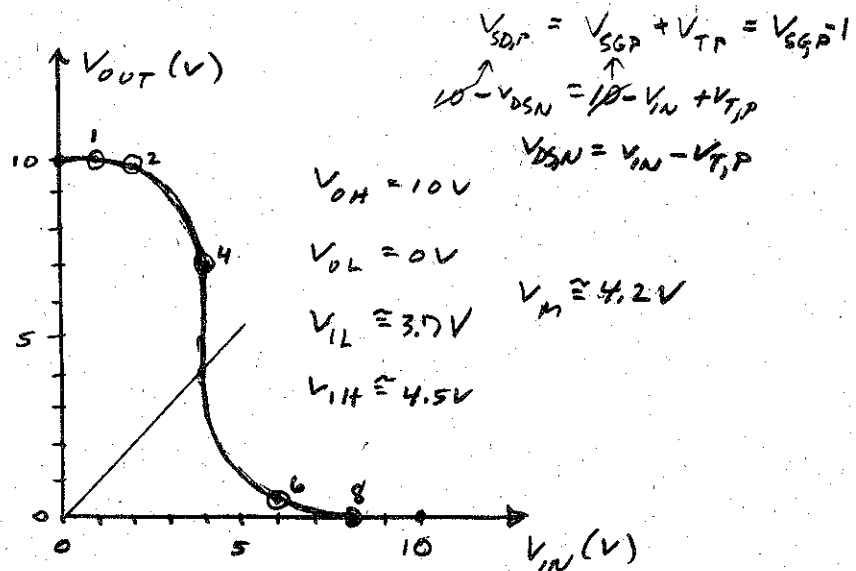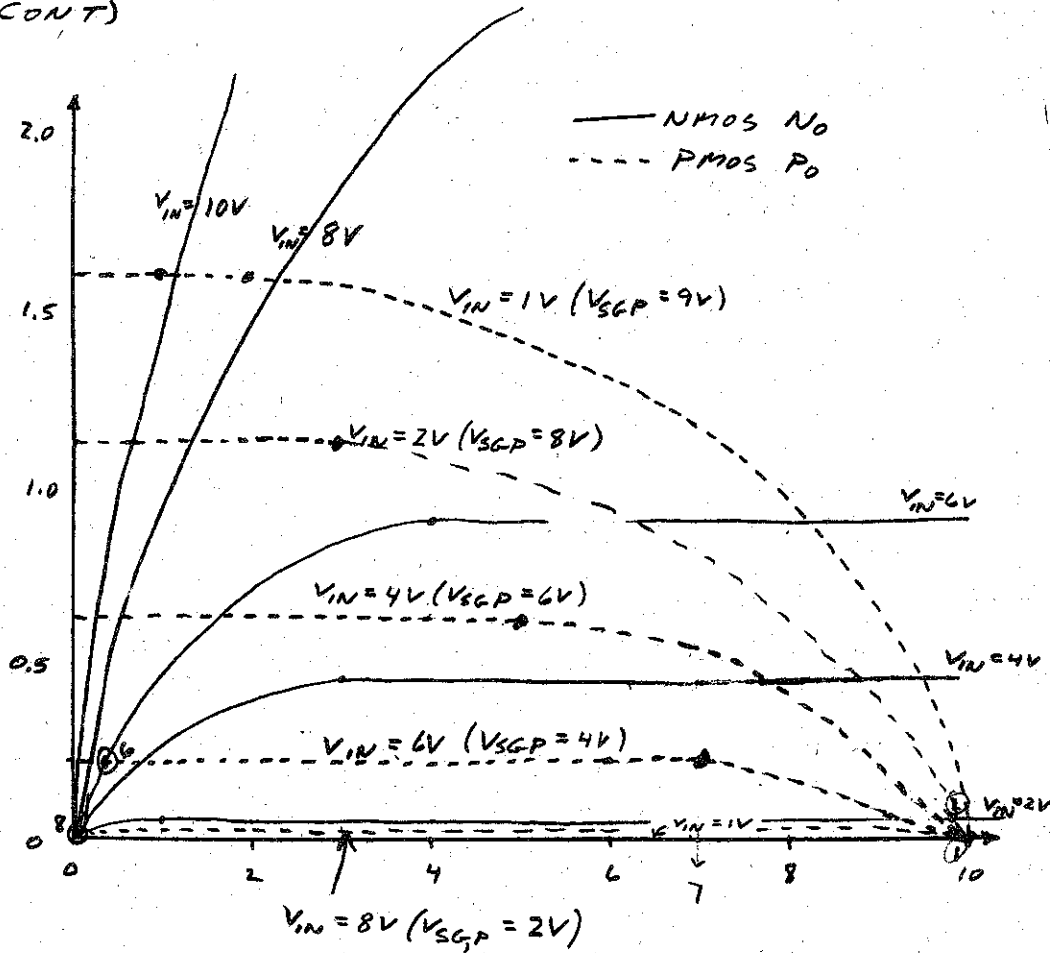

CHAPTER 24 (CONT)

24.11 BY INSPECTION OF THE CIRCUIT

$$F = \overline{AB} + \overline{AB} = (\overline{A+B})(A+B) = \overline{A}\overline{B} + AB \quad \text{XNOR}$$

24.12 XOR

24.13 THE RELATION FOR W/L RATIOS FOR CMOS NAND GATES WITH m INPUTS IS

$$2.5 \left(\frac{W}{L} \right)_N = \left(\frac{W}{L} \right)_P$$

THUS, FOR A 2 INPUT NAND gate

$$\frac{2.5}{2} \left(\frac{W}{L} \right)_N = \left(\frac{W}{L} \right)_P$$

CASE A: CHOOSE MINIMUM SIZE NMOSFET

$$\left(\frac{W}{L} \right)_N = \frac{4\mu\text{m}}{2\mu\text{m}}$$

AND THUS

$$\left(\frac{W}{L} \right)_P = \left(\frac{4\mu\text{m}}{2\mu\text{m}} \right) \left(\frac{2.5}{2} \right) = \frac{5\mu\text{m}}{2\mu\text{m}}$$

FOR THIS CASE THE CHIP AREA FOR THE 4 TRANSISTORS IS

$$\text{AREA} = 2 (A_N + A_P) = 2 (4 \times 2 + 5 \times 2) = 36 \mu\text{m}^2$$

CASE B CHOOSE MINIMUM SIZE PMOSFETS

$$\left(\frac{W}{L} \right)_P = \frac{4\mu\text{m}}{2\mu\text{m}}$$

THUS,

$$\left(\frac{W}{L} \right)_N = \left(\frac{4}{2} \right) \left(\frac{2}{2.5} \right) = \frac{4\mu\text{m}}{2.5\mu\text{m}} = \frac{3.2\mu\text{m}}{2\mu\text{m}}$$

AND

$$\text{AREA} = 2 (4 \times 2 + 3.2 \times 2) = 28.8 \mu\text{m}^2$$

CHAPTER 25 SOLUTIONS (CONT'D)

25.6)

	V_{IN}	N	P	PULL-UP PATH	PULL-DOWN PATH	V_{OUT}
1	LOW	OFF	ON	YES	NO	HIGH
2	HIGH	ON	OFF	NO	YES	LOW
3	Z	?	?	NO	NO	Z
4	X	?	?	YES	YES	X

25.7) EQUATE THE LINEAR DRAIN CURRENTS FOR THE N- AND P- CHANNEL MOSFETS:

$$I_{D,N} (LIN) = I_{D,P} (LIN)$$

$$k_N [(V_{GS,N} - V_{TN}) V_{DS,N} - \frac{V_{DS,N}^2}{2}] = k_P [(V_{SG,P} + V_{TP}) V_{SD,P} - \frac{V_{SD,P}^2}{2}]$$

SUBSTITUTE:

$$V_{GS,N} = V_{IN} = V_{OH} = 5V$$

$$V_{SG,P} = V_{DD} - V_{IN} = V_{DD} - V_{OL} = 5V$$

$$V_{DS,N} = V_{OUT}$$

$$V_{SD,P} = V_{DD} - V_{OUT}$$

$$80\mu [(5 - 1)V_{OUT} - \frac{V_{OUT}^2}{2}] = 80\mu [(5 + (-1))(5 - V_{OUT}) - \frac{(5 - V_{OUT})^2}{2}]$$

$$4V_{OUT} - \frac{V_{OUT}^2}{2} = 20 - 4V_{OUT} - \frac{25}{2} + 5V_{OUT} - \frac{V_{OUT}^2}{2} \rightarrow 3V_{OUT} = 20 - \frac{25}{2} = 7.5$$

(COLLECT LIKE TERMS AND SOLVE FOR V_{OUT} ;

$$V_{OUT} = 2.5V = V_X$$

25.8


V_A	$V_B = V_C$	V_{OUT}
LOW	LOW	V_{DD}
LOW	H _i	LOW
H _i	LOW	LOW
H _i	H _i	LOW

25.9

V_{IN}	$\overline{V_{PEN}}$	V_{NEN}	V_{TINV}
LOW	LOW	LOW	H _i
LOW	LOW	H _i	H _i
LOW	H _i	LOW	X
LOW	H _i	H _i	X
H _i	LOW	LOW	X
H _i	LOW	H _i	LOW
H _i	H _i	LOW	X
H _i	H _i	H _i	LOW

CHAPTER 15 (CONT)

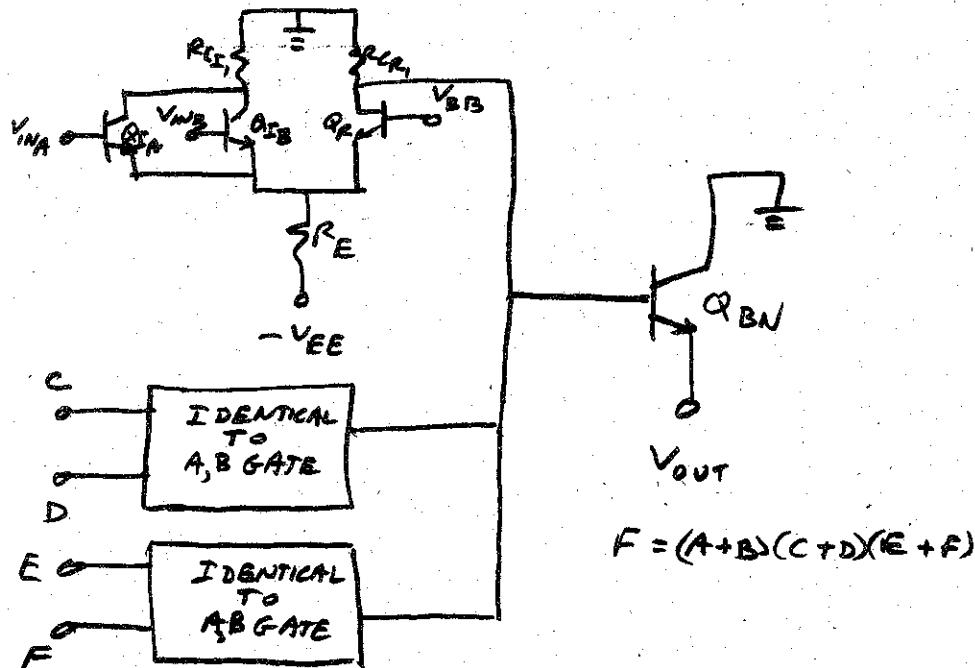15.11 REALIZE THE LOGIC FUNCTION $F = (A+B)(C+D)(E+F)$



15.12 TO OBTAIN THE INVERSE OF F , FROM PROBLEM 15.11, $\bar{F} = \overline{(A+B)(C+D)(E+F)}$ USE SAME CIRCUIT AS PROBLEM 15.11 EXCEPT COLLECTOR DOTTING OF INPUT TRANSISTOR COLLECTORS WITH OUTPUT BUFFER BJT Q_{BINV} .

15.13

A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

15.14

A	B	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

CHAPTER 26 SOLUTIONS (CONT.)

26.10 TWICE THE DRIVE STRENGTH IMPLIES THAT THE W/L RATIOS OF THE DEVICES IN THE STACK SHOULD BE DOUBLED. THUS,

$$\frac{W_{ND}}{L_{ND}} = \frac{W_{NE}}{L_{NE}} = 2 \left(\frac{8 \mu\text{m}}{2 \mu\text{m}} \right) = 8$$

AND

$$\frac{W_{PD}}{L_{PD}} = \frac{W_{PE}}{L_{PE}} = 2 \left(\frac{20 \mu\text{m}}{2 \mu\text{m}} \right) = 20$$

HENCE

$$R_{NI} = R_{ND} = R'_{NE} \frac{W_{NE}}{L_{NE}} = 40 \mu\text{A/V}^2 = 320 \mu\text{A/V}^2$$

$$R_{PI} = R_{PD} = R'_{PE} \frac{W_{PE}}{L_{PE}} = 16 \mu\text{A/V}^2 = 320 \mu\text{A/V}^2$$

ALSO

$$\frac{W_{NF}}{L_{NF}} = \left[\frac{V_{ID} - V_{TN}}{V_{DD} - V_{ID}} \right]^2 \frac{W_{NE}}{L_{NE}} = \left[\frac{4 - 1}{5 - 4} \right]^2 8 = 72$$

$$\frac{W_{PF}}{L_{PF}} = \left[\frac{V_{DD} + V_{TP} - V_{IN}}{V_{IN}} \right]^2 \frac{W_{PE}}{L_{PE}} = \left[\frac{5 - 1 - 1}{1} \right]^2 20 = 180$$

26.11 USING THE EQS OF THE PREVIOUS PROBLEM (26.10)

$$\frac{W_{ND}}{L_{ND}} = \frac{W_{NE}}{L_{NE}} = 2 \frac{8 \mu\text{m}}{2 \mu\text{m}} = 8 \text{ AND } \frac{W_{PD}}{L_{PD}} = \frac{W_{PE}}{L_{PE}} = 2 \frac{20 \mu\text{m}}{2 \mu\text{m}} = 20$$

$$\frac{W_{NF}}{L_{NF}} = \left[\frac{4 - 1}{7 - 4} \right]^2 8 = 8$$

$$\frac{W_{PF}}{L_{PF}} = \left[\frac{7 - 1 - 1}{1} \right]^2 20 = 25(20) = 500$$

26.12 USING THE EQS OF THE PREVIOUS PROBLEMS

SAME RESULTS FOR N_D, P_D, N_E, P_E . THEN

$$\frac{W_{NF}}{L_{NF}} = \left[\frac{4 - 1}{10 - 4} \right]^2 8 = \left[\frac{1}{4} \right]^2 8 = 2$$

$$\frac{W_{PF}}{L_{PF}} = \left[\frac{10 - 1 - 1}{1} \right]^2 20 = 64(20) = 1280$$

CHAPTER 27 (CONT)

27.4 (CONT)

For the third stage:

$$k_{N_3} = k_{P_3} = k'_N (W/L)_{N_3} = 40 \mu (120/2) = 2.4 \text{ mA/V}^2$$

$$C_{L_3} = [(W/L)_{N_4} + (W/L)_{P_4}] C_{ox} = [1750 \times 2 + 700 \times 2] 690 \text{ a} \\ = (3500 + 1400) 690 = 3.38 \text{ pF}$$

$$\tau_{P_3} = A_{CL_3} / k_{P_3} = \frac{0.322 \times 3.38 \text{ p}}{2.4 \text{ m}} = 0.45 \text{ ms}$$

For the Fourth stage:

$$k_{N_4} = k_{P_4} = (40 \mu)(700/2) = 14 \text{ mA/V}^2$$

$$C_{L_4} = C_L = 5 \text{ pF}$$

$$\tau_{P_4} = \frac{0.322 (5 \text{ p})}{14 \text{ m}} = 0.115 \text{ ms}$$

$$\tau_{P_{TOTAL}} = 0.39 + 0.47 + 0.45 + 0.115 = 1.425 \text{ ms}$$

27.5 ALL k_N and $k_P \times \frac{1000}{690}$ and ALL $C_{IN} \times \frac{1000}{690}$

\therefore ALL τ unchanged except τ_4

27.6 Transconductance Parameters doubled
From Problem 27.4:

$$A=B=0.322 \text{ V}, k_{P_1} = 160 \text{ mA/V}^2, C_{L_1} = 96.6 \text{ fF}$$

$$\tau_{P_1} = \frac{0.322 (96.6 \text{ f})}{160 \mu} = \frac{0.39}{2} = 0.195 \text{ ms}$$

For the second stage

$$\tau_{P_2} = A_{CL_2} / k_{P_2} = 0.47/2 = 0.235 \text{ ms}$$

For the 3rd stage

$$\tau_{P_3} = A_{CL_3} / k_{P_3} = 0.45/2 = 0.225 \text{ ms}$$

$$\text{For the 4th stage } \tau_{P_4} = \frac{0.115}{2} = 0.0575 \text{ ms}$$

$$\therefore \tau_{TOTAL} = 0.7125 \text{ ms}$$

CHAPTER 34 (CONT)

PRODUCED DUE TO THE LARGE GATE CURRENT,
THE FANOUT AND RELIABILITY OF THE GATE
ALSO BECOME UNACCEPTABLE.

34.6

$$\begin{aligned} a &= 0.1 \mu\text{m} \\ W &= 0.6 \mu\text{m} \\ L &= 3.0 \mu\text{m} \end{aligned}$$

$\beta' =$ PROCESS TRANSCONDUCTANCE
 $\beta =$ DEVICE TRANSCONDUCTANCE

$$\beta' = \frac{\mu N \epsilon_{\text{GaAs}}}{2a} = \frac{8600 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} \times 1.16 \times 10^{-12} \text{ F/cm}}{2 \times 10^{-5} \text{ cm}}$$

$$\therefore \beta' = 498.8 \mu\text{A/V}^2 \approx 500 \mu\text{A/V}^2$$

$$\beta = \beta' W / L = 498.8 \times \frac{0.6}{3.0} = 99.76 \mu\text{A/V}^2$$

$$\therefore \beta = 99.76 \mu\text{A/V}^2 \approx 100 \mu\text{A/V}^2$$

34.7

$$V_p = \frac{q N_D a^2}{2 \epsilon_{\text{GaAs}}}$$

$$N_D = 10^{17} / \text{cm}^3$$

$$= \frac{1.6 \times 10^{-19} \times 10^{17} \times 10^{-5}}{2 \times 1.16 \times 10^{-12}}$$

$$V_p = 0.69 \text{ V}$$

$$\begin{aligned} V_T &= V_{bi} - V_p \\ &= 0.8 - 0.69 \\ &= 0.11 \text{ V} \end{aligned}$$

$$V_T = 0.11 \text{ V}$$

CHAPTER 35 (CONT)

35.7

a) $V_{OH} = V_{SBD, GaAs} (ON) = 0.8 \text{ V}$

$V_{OH} = 0.8 \text{ V}$

$$V_{IL} = V_{T,0} + |V_{T,L}| \left[\frac{\beta_L [1 + \lambda_L (V_{DD} - V_{SBD, GaAs})] \tanh \alpha_L (V_{DD} - V_{SBD, GaAs})}{\beta_0 (1 + \lambda_0 V_{SBD, GaAs}) \tanh \alpha_0 V_{SBD, GaAs}} \right]^{1/2}$$

$$= 0.2 + 1.1 \left[\frac{1}{10} \frac{\tanh 2(0.2)}{\tanh 2(0.8)} \right]^{1/2} = 0.2 + 0.2$$

$V_{IL} = 0.4 \text{ V}$

$$V_{OL} = \frac{1}{\alpha_0} \cdot \frac{\beta_L}{\beta_0} \frac{V_{T,L}^2}{(V_{OH} - V_{T,0})^2} \cdot (1 + \lambda_L V_{DD}) = \frac{1}{2} \frac{1}{10} \frac{(-1)^2}{(0.8 - 0.2)^2}$$

$V_{OL} = 0.139 \text{ V} = 0.14 \text{ V}$

FOR DETERMINATION OF V_{IH} , NUMERICAL SOLUTION OF TWO EQUATIONS, AS IN PROBLEM 35.2, IS REQUIRED. STARTING WITH A GUESS VALUE FOR EACH OF V_{IN} I.E. V_{IH} AND V_{OUT} , SOLUTION CAN BE WORKED OUT ON MATHCAD.

$V_{OUT} = 0.22 \text{ V}$

$V_{IH} = 0.69 \text{ V}$ SEE NEXT PAGE FOR DETAILS

$V_{NMH} = V_{OH} - V_{IH} = 0.11 \text{ V}$

$V_{NML} = V_{IL} - V_{OL} = 0.26 \text{ V}$

b) DIRECT SUBSTITUTION INTO THE EXPRESSIONS AS IN 35.5 GIVES

$I_{DD} (OH) = 88.535 \text{ } \mu\text{A} \leftarrow \frac{\beta_L V_{T,L}^2 (1 + \lambda_L (V_{DD} - V_{OH})) \tanh \alpha_L (V_{DD} - V_{OH})}{100 (-1)^2 (1 + 0.1(0.7)) \tanh 2(0.7)}$

$I_{DD} (OL) = 99.14 \text{ } \mu\text{A} \leftarrow 100 (1)^2 \tanh 2(1.5 - 0.14)$

$P_{DD} = \frac{(88.535 + 99.14)}{2} \cdot (1.5)$

$P_{DD} = 140.8 \text{ } \mu\text{W}$


CHAPTER 35 (CONT)

35.7

Determination of V_{IH}

$$(1) V_{IH} = 0.2 + \frac{1}{10 \tanh 2V_{out}}$$
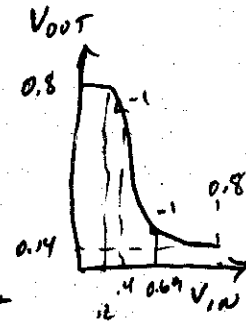
$$(2) V_{IH} = 0.2 + \cosh^2 2V_{out} \tanh 2V_{out}$$



Equates

$$0.316 = \frac{1}{V_{IO}} = \cosh^2 2V_{out} \tanh^3 2V_{out}$$

choose $2V_{out}$	calculate $\cosh^2(2V_{out}) (\tanh^3(2V_{out})) =$
0.22	$(1.0492) (1.007) = 0.1$
0.4	$(1.169) (0.234) = 0.274$
0.38	$(1.151) (0.218) = 0.25$
0.5	$(1.271) (0.314) = 0.4$
0.45	$(1.217) (0.274) = 0.33$
0.44	$(1.21) (0.266) = 0.32$

$$\therefore 2V_{OUT} \approx 0.44 V \rightarrow V_{OUT} = 0.22$$

$$V_{IH} = 0.2 + \cosh^2(0.44) \tanh(0.44)$$

$$= 0.2 + \underbrace{(1.206)(0.41)}_{0.49} = \underline{0.69 V}$$

as a check

$$V_{IH} = 0.2 + \frac{1}{\sqrt{10 \tanh 0.44}} = 0.2 + .49 = 0.69$$

c) MAXIMUM FANOUT CHAPTER 35 (CONT)

MAXIMUM FANOUT IS OBTAINED FOR $V_{OUT} = V_{IH}$

$$I_{D,L} = \beta_L V_{T,L}^2 \cdot \tanh(\alpha_L (V_{DD} - V_{IH})) (1 + \lambda_L (V_{DD} - V_{IH}))$$

$$= 92.34 \mu A$$

$$I_{G'o(IH)} = I_{SBD} \cdot \exp\left[\frac{V_{IH}}{0.026}\right] = (10^{-12} A) \left(\exp\left[\frac{0.69}{0.026}\right]\right)$$

$$= 0.335 \mu A$$

$$N = \frac{I_{D,L}}{I_{G'o(IH)}} = 275.64$$

$$N_{MAX} = 275$$

FANOUT FOR $N_{MH} = 0.1 V$

$$V_{OUT} = V_{IH} + N_{MH}$$

$$V_{OUT} = 0.79$$

$$I_{D,L}(V_{OUT}=0.79) = \beta_L V_{T,L}^2 \cdot \tanh[\alpha_L (V_{DD} - V_{OUT})] (1 + \lambda_L (V_{DD} - V_{OUT}))$$

$$= 88.809 \mu A$$

$$I_{G'o(V_{OUT}=0.794)} = I_{SBD} \cdot \exp(V_{OUT}/0.026)$$

$$= 15.6 \mu A$$

$$N = I_{D,L} / I_{G'o}$$

$$= 5.69$$

$$N = 5$$

CHAPTER 36 (CONT)


$$V_{IH} = 1.4 + (0.32) \tanh^{-1/2}(0.426)$$

$$= 1.4 + 0.5$$

$$V_{IH} = 1.9 \text{ V}$$

$$V_{NML} = V_{IL} - V_{OL} = 1.4 - 0.05 = 1.35 \text{ V}$$
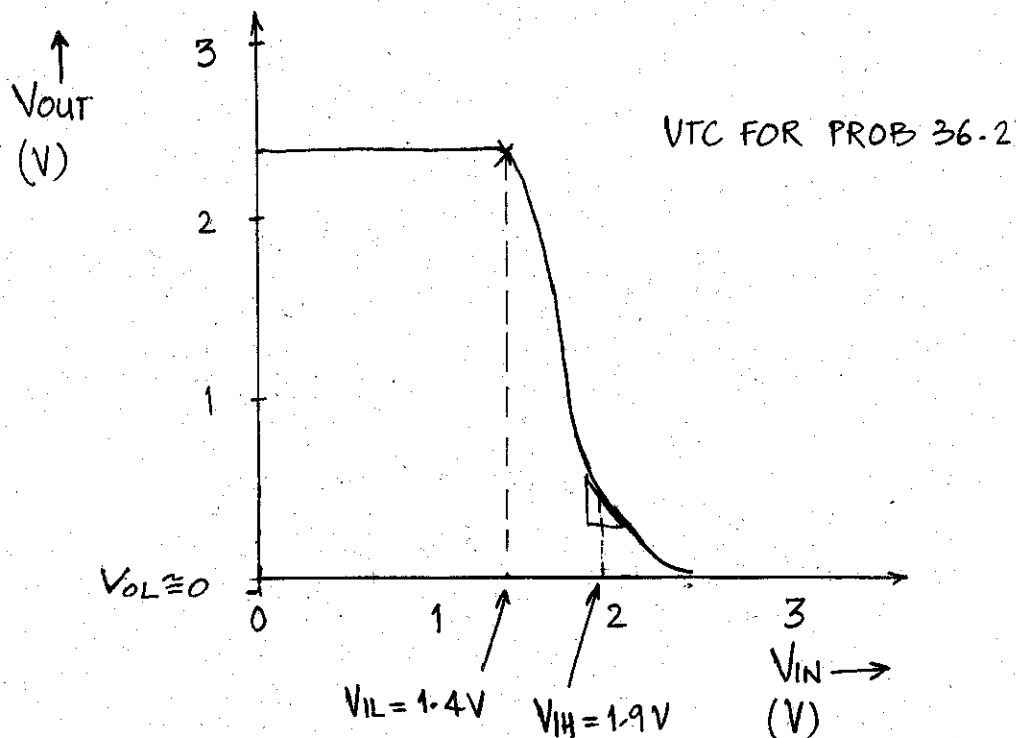
$$V_{NMH} = V_{OH} - V_{IH} = 2.4 - 1.9 = 0.5 \text{ V}$$



36.3

AVERAGE POWER DISSIPATION

$$P_{DISS} = I_{DD} \cdot V_{DD} + I_{SS} \cdot V_{SS}$$

$$\text{WHERE } I_{DD} = \frac{I_{DD(OH)} + I_{DD(OL)}}{2}$$

$$I_{SS} = \frac{I_{SS(OH)} + I_{SS(OL)}}{2}$$

CHAPTER 36 (CONT)

36.3 (CONT)

$$I_{D0L} = I_{D0L} = \beta_L V_{T,L}^2 (1 + \lambda_L (V_{DD} - V_{OL}))$$

$$= \left(\frac{100}{10}\right) (-1)^2 (1 + 0.2 (3 - 0.05))$$

$$= 10 (1 + 0.59) = \underline{15.9 \mu A}$$

$$I_{D0H} = \beta_L V_{T,L}^2 (1 + \lambda_L V_{DS,L}) \tanh \lambda_L V_{SS,L}$$

$$= \left(\frac{100}{10}\right) (-1)^2 (1 + 0.2 (3 - 2.4)) \tanh \underbrace{2 (3 - 2.4)}_{0.83}$$

$$= 10 (1 + 0.12) (0.83)$$

$$= \underline{9.3 \mu A}$$

$$I_{SS0L} = \beta_D V_{T,D}^2 (1 + \lambda_D (V_{OL} - 3 V_{SBD+MIS}^{(ON)} + V_{SS}))$$

$$= 100 (-1)^2 (1 + 0.2 (2.4 - 2.4 - (-3)))$$

$$= 100 (1 + 0.6) = \underline{160 \mu A}$$

$$I_{SS0H} = \beta_D V_{T,D}^2 (1 + \lambda_D (V_{OL} - 3 V_{SBD+MIS}^{(ON)} + V_{SS})) \tanh \lambda_D V_{SS,L}$$

$$= 100 (-1)^2 (1 + 0.2 (0.05 - 2.4 + 3)) \tanh 2 (0.65)$$

$$= 100 (1 + 0.2 (0.65)) (0.86) = \underline{97.2 \mu A}$$

$$P_{DSS} (AV) = V_{DD} I_{DD} + V_{SS} I_{SS} = 3 \left(\frac{15.9 + 9.3}{2} \right) + 3 \left(\frac{160 + 97.2}{2} \right)$$

$$= 37.8 + 386 = 423.8 \mu W$$

$$= 0.42 mW$$

$$37.4 \quad V_{OH} = V_{DD} - 3V_{SBD, GaAs(ON)} = \boxed{0.6V}$$

$$a) \quad V_{IL} = V_{T,0} = \boxed{-1.5V}$$

$$V_{OL} = -3V_{SBD, GaAs(ON)} = \boxed{-2.4V}$$

THE FOLLOWING EXPRESSIONS ARE NUMERICALLY SOLVED FOR V_{IH}

$$\beta_L V_{T,L}^2 \tanh \alpha_L V_{DS,L} \cong \beta_0 (V_{IN} - V_{T,0})^2 \tanh \alpha_0 V_{DS,0} + \beta_C V_{T,C}^2 - \beta_F (V_{GS,F} - V_{T,F})^2$$

AND

$$\frac{\alpha_L V_{T,L}^2}{\cosh^2 \alpha_L V_{DS,L}} + \frac{(\beta_0/\beta_L) \alpha_L (V_{IN} - V_{T,0})^2}{\cosh^2 \alpha_0 V_{DS,0}} = \frac{2 \beta_0 (V_{IN} - V_{T,0}) \tanh \alpha_0 V_{DS,0}}{\beta_L}$$

$$\text{WHERE } V_{DS,L} = V_{DD} - [V_{OUT} + 3V_{SBD, GaAs(ON)}]$$

$$V_{DS,0} = V_{OUT} + 3V_{SBD, GaAs(ON)}$$

WE GET,

$$V_{OUT} = -1.95V$$

AND

$$\boxed{V_{IH} = -0.05V}$$

SEE NEXT PAGE

AND,

$$V_{NMH} = V_{OH} - V_{IH} \quad \text{AND} \quad V_{NML} = V_{IL} - V_{OL}$$

$$V_{NMH} = 0.65V$$

$$V_{NML} = -1.5 + 2.4 = 0.9V$$

$$b) \quad I_{SS(OL)} = \frac{(100)}{\beta_C} \cdot \frac{(1.5)^2}{V_{T,C}^2} \left[1 + \frac{(0)}{\lambda_C} (V_{OL} + V_{SS}) \right] \cdot \tanh \left[\frac{\alpha_C (V_{OL} + V_{SS})}{2(-2.4 + 3)} \right]$$

$$= 187.6 \mu A$$

$$I_{SS(OH)} = \frac{(100)}{\beta_C} \cdot \frac{(1.5)^2}{V_{T,C}^2} \left[1 + \frac{(0)}{\lambda_C} (V_{OH} + V_{SS}) \right] \cdot \tanh \left[\frac{\alpha_C (V_{OH} + V_{SS})}{2(0.6 + 3)} \right]$$

$$= 225 \mu A$$

$$I_{SS} = (I_{SS(OL)} + I_{SS(OH)})/2 = 206.3 \mu A$$

$$I_{DD(OL)} = I_{D,L(OL)} + I_{D,F(OL)}$$

$$= \frac{\beta_L V_{T,L}^2}{50} \frac{(1.5)^2}{V_{T,L}^2} (1 + \lambda_L V_{DD}) \cdot \tanh \alpha_L V_{DD} + \frac{(0.8 + 1.5)^2}{50} \beta_F (V_{GS,F} - V_{T,F})^2$$

$$\left\{ 1 + \lambda_F V_1 \right\} \cdot \tanh \alpha_F V_1$$

$$= 377 \mu A$$

WHERE $V_1 = V_{DD} + V_{SBD, GaAs(ON)}$

$$I_{DD(OH)} = I_{SS(OH)} = 225 \mu A$$

$$I_{DD} = (I_{DD(OL)} + I_{DD(OH)})/2 = 301 \mu A$$

$$P_{DISS} = V_{DD} \cdot I_{DD} + V_{SS} \cdot I_{SS} = \boxed{1.522 mW}$$

CHAPTER 37 (CONT)

37.4 (CONT)

V_{IH} : 2 EQUATIONS

$$(1) \quad \cancel{50} (-1.5)^2 \tanh^2(0.6 - V_{OUT}) = \cancel{100} (V_{IN} + 1.5)^2 \tanh^2(V_{OUT} + 2.4) + \cancel{100} (1.5)^2 - \cancel{50} (0.8 + 1.5)^2$$

$$(-1.5)^2 = 2(V_{IN} + 1.5)^2 \tanh^2(V_{OUT} + 2.4) + 2(2.25) - (2.3)^2$$

$$2.25 - 4.5 + 5.25 = 2(V_{IN} + 1.5)^2 \tanh^2(x)$$

$$3 = 2(V_{IN} + 1.5)^2 \tanh^2(x)$$

$$(1) \quad V_{IN} + 1.5 = \sqrt{\frac{3}{2} \frac{1}{\tanh^2(x)}} = \frac{1.225}{\tanh^{1/2}(x)}$$

$$(2) \quad \frac{2(-1.5)^2}{\cosh^2(2(0.6 - V_{OUT}))} + \frac{\cancel{100} 2(V_{IN} + 1.5)^2}{\cosh^2(2(V_{OUT} + 2.4))} = 2 \left(\frac{100}{50} \right) (V_{IN} + 1.5) \tanh(x)$$

$$\stackrel{\approx 0}{=} (2) \quad V_{IN} + 1.5 = \cosh^2 x \tanh x$$

$$\text{where } x = 2(V_{OUT} + 2.4)$$

$$\text{Equate (1) \& (2)} \quad \frac{1.225}{\tanh^{1/2} x} = \cosh^2 x \tanh x$$

$$\text{or } 1.225 = \cosh^2 x \tanh^{3/2} x$$


CHOOSE x	Calculate $\cosh^2 x \tanh^{3/2} x$
1	$2.381 \times 0.665 = 1.58$
0.85	$1.914 \times 0.574 = 1.1$
0.9	$2.054 \times 0.6 = 1.25$ close enough

$$\therefore x = 0.9 = 2(V_{OUT} + 2.4) \rightarrow V_{OUT} = -1.95V$$

Back substitution

$$V_{IN} + 1.5 = \frac{1.225}{\tanh^{1/2}(0.9)} \rightarrow V_{IN} = -1.5 + 1.45 = -0.05V$$

37.4

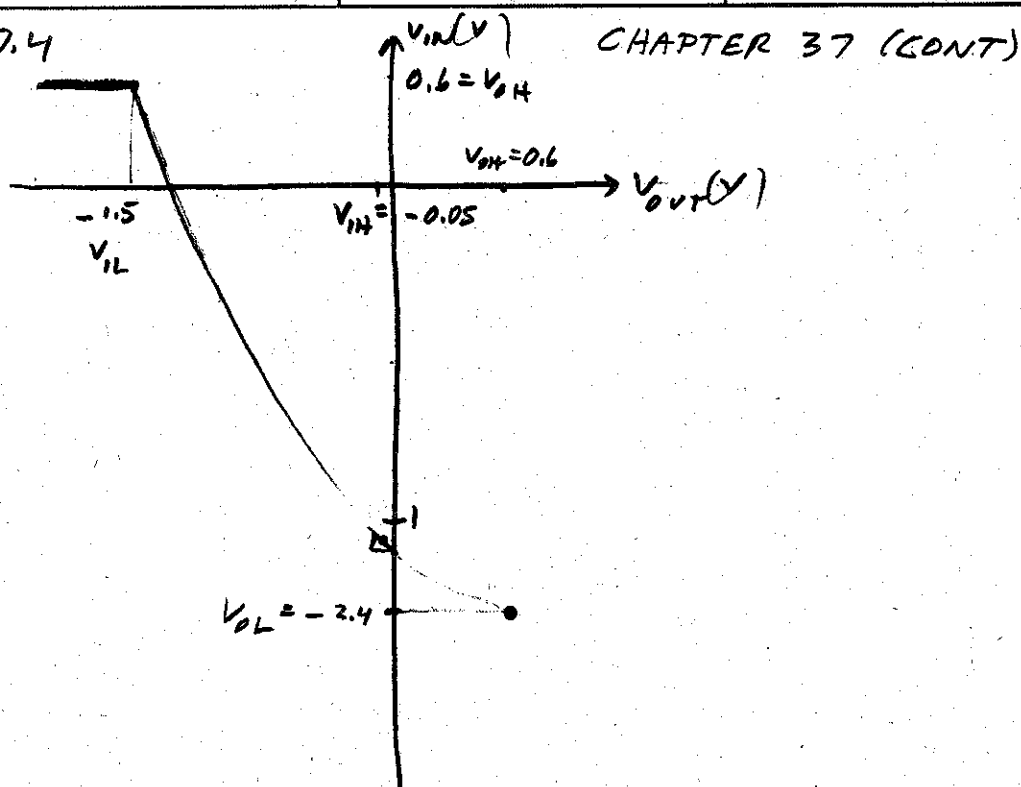

$$37.5 \quad V_{OH} = V_{DD} - 3V_{SBD, G\Delta AS(ON)} = 0.6 \text{ V}$$

$$V_{IL} = V_{T,D} = -1.5 \text{ V}$$

$$V_{OL} = -3V_{SBD, G\Delta AS(ON)} = -2.4 \text{ V}$$

THE EQS TO SOLVE ARE:

$$\beta_L V_{T,L}^2 \tanh \alpha_L V_{DS,L} \approx \beta_O (V_{IN} - V_{T,O})^2 \tanh \alpha_O V_{DS,O} + \beta_C V_{T,C}^2 - \beta_F (V_{GS,F} - V_{T,O})^2$$

and

$$\frac{\alpha_L V_{T,L}^2}{\cosh^2 \alpha_L V_{DS,L}} + \frac{\frac{\beta_O}{\beta_L} \alpha_L (V_{IN} - V_{T,O})^2}{\cosh^2 \alpha_O V_{DS,O}} = 2 \frac{\beta_O}{\beta_L} (V_{IN} - V_{T,O}) \tanh \alpha_O V_{DS,O}$$

$$\text{where } V_{DS,L} = V_{DD} - (V_{OUT} + 3V_{SBD, G\Delta AS(ON)})$$

$$\text{and } V_{DS,O} = V_{OUT} + 3V_{SBD, G\Delta AS(ON)}$$

Substituting into the EQS YIELDS

$$500(1.5)^2(1) = 1000(V_{IN} + 1.5)^2 \tanh 2V_{DS} + 100(1.5)^2 - 100(0.6 + 1.5)^2 \quad (1)$$

and

$$\frac{1000}{500} \frac{2(V_{IN} + 1.5)^2}{\cosh^2 2(V_{OUT} + 2.4)} = 2 \left(\frac{1000}{500} \right) (V_{IN} + 1.5) \tanh 2(V_{OUT} + 2.4) \quad (2)$$

CHAPTER 39 (SOLUTIONS)

39.1 ANALYZE THE CIRCUIT TO SEE THAT

$$V_{out} = \text{HIGH FOR } V_{inA} = \text{HIGH OR } V_{inB} = \text{HIGH}$$

ALSO, WHEN $V_{inA} = V_{inB} = \text{HIGH}$, $V_{out} = \text{HIGH}$
and $V_{out} = \text{LOW FOR } V_{inA} = V_{inB} = \text{LOW}$

THIS GATE PERFORMS XOR

39.2 BY INSPECTION OF THE FIGURE, THE LOGIC
OUTPUT IS $\overline{(A+C)(B+D)}$

$$V_{OH} = V_{DD}, \quad V_{OL} = 2V_{OL}(\text{ONE MESFET})$$

Yes, Fig 39.9

39.3 BY INSPECTION OF THE FIGURE, THE LOGIC
OUTPUT IS $\overline{AB+CD}$

$$V_{OH} \approx V_{DD} - 3V_{SD(ON)}$$

$$V_{OL} = 2V_{OL}(\text{ONE MESFET})$$

39.4

OUTPUT IS $\overline{A+B}$

39.5

OUTPUT IS $\overline{A \cdot B}$

CHAPTER 30 SOLUTIONS (CONT)

30.4 a) STATIC POWER DISSIPATION

$$P_{DISS} = I_{DD} V_{DD}$$

OUTPUT HIGH STATE : N_0 (OFF) $\Rightarrow I_{DD}(OH) = 0$

OUTPUT LOW STATE : P_0 (OFF) $\Rightarrow I_{DD}(OL) = 0$

$$\therefore I_{DD} = \frac{I_{DD}(OH) + I_{DD}(OL)}{2} = 0$$

$$P_{DISS} = 0$$

b) DYNAMIC POWER DISSIPATION

$$P_{DD} = C_L \nu V_{DD}^2 = 0.08 \times 10^{-12} \times 50 \times 10^6 \times 5^2$$

$$P_{DD} = 100 \mu W, \text{ Total Power Diss} = 100 \mu W$$


30.5 $V_{IN}(\text{LOW})$; N_1 (OFF), P_1 (ON), Q_N (OFF), Q_P (SAT)

$$V_{OUT} = V_{DD} - V_{CE,P(\text{SAT})} = V_{OH} = 10 - 0.2 = 9.8V$$

$V_{IN}(\text{HIGH})$; N_1 (ON), P_1 (OFF), Q_P (OFF), Q_N (SAT)

$$V_{OUT} = V_{CE,N(\text{SAT})} = V_{OL} = 0.2V$$

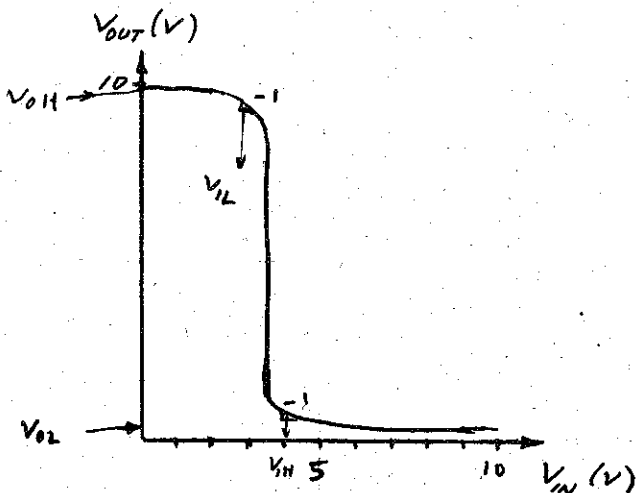TO FIND V_{IL} & V_{IH} USE TEXT PROCEDURE



CHAPTER 30 SOLUTIONS (CONT)

30.6 a) STATIC POWER DISSIPATION

$$P_{DISS} = I_{DD} V_{DD}$$

$$I_{DD} = \frac{I_{DD(04)} + I_{DD(02)}}{2} = \frac{0 + 0}{2} = 0$$

$$P_{DISS} = 0 \text{ REGARDLESS OF } V_{DD} \text{ VALUE}$$

b) DYNAMIC POWER DISSIPATION

$$P_{DD} = C_L \Delta V_{DD}^2 = 0.05 \times 10^{-12} \times 25 \times 10^6 \times 10^2$$

$$P_{DD} = 125 \mu W$$

$$\text{Total Power DISS} = 125 \mu W$$

30.7 $V_{IN}(\text{LOW})$; $N_I(\text{OFF})$, $P_I(\text{ON})$, $Q_N(\text{ON})$, $Q_P(\text{OFF})$

Q_N GIVES LARGE CURRENT INITIALLY

$$V_{OUT} = V_{DD} - V_{BE,N}(\text{FA}) = V_{OH} = 5 - 0.7 = 4.3V$$

$V_{IN}(\text{HIGH})$; $P_I(\text{OFF})$, $N_I(\text{ON})$, $Q_N(\text{OFF})$, $Q_P(\text{ON})$ - PROVIDES PULL-DOWN

$$V_{OUT} = V_{BE,P}(\text{FA}) = V_{OL} = 0.7V$$

$$\text{LOGIC SWING} = V_{DD} - 2V_{BE}(\text{FA}) = 5 - 2(0.7) = 3.6V$$

30.8 STATIC POWER DISSIPATION = $I_{DD} V_{DD} = 0$ ($V_{DD} = 0$)

30.9 V_{OH} IS $V_{DD} - V_{BE,N_2}(\text{FA}) = 5 - 0.7 = 4.3V$ (N_3 AND P_2 ON)

$$V_{OL} \text{ IS } V_{BE,N_1}(\text{FA}) = 0.7V \text{ (} N_1 \text{ IS ON \& } N_2 \text{ OFF)}$$

30.10 STATIC POWER DISSIPATION = 0

30.11 $V_{OH} = V_{DD}$, $V_{OL} = 0$

30.12 STATIC POWER DISSIPATION = 0